



BEL ECE Q&A SET 6

Q. 1) Simplify the expression $\overline{AB} + \bar{A} + AB$

(a) = 1

(b) = 0

(c) = A

(d) = \bar{A}

ANS: B

Applying De-Morgan's law in the above expression can be written as:

$$F = \overline{\overline{AB}} \cdot \overline{\bar{A}} \cdot \overline{AB}$$

$$F = AB \cdot A \cdot (\bar{A} + \bar{B})$$

$$F = AB(\bar{A} + \bar{B})$$

$$F = A\bar{B} + A\bar{B}$$

$$F = 0$$

Q. 2) Find the average value of the current , $I(t) = 10 + 10\pi \sin 314t$

(a) 200 Amp

(b) 10 Amp

(c) 0 Amp

(d) 30 Amp

ANS: B

The average of the sine wave is 0A.

The RMS value of the sine wave is given by:

$$\text{RMS} = \frac{A}{\sqrt{2}}$$

where, A is the max value of the sine signal

Calculation:

Given, $i = (10 + 10\pi \sin 314t)$ A

$$i_{\text{avg}} = (\text{DC})_{\text{avg}} + (\text{AC})_{\text{avg}}$$

$$i_{\text{avg}} = 10 + 0$$

$$i_{\text{avg}} = 10 \text{ A}$$

Q. 3) Maxwell's third equation is derived from _____.

- (a) Ampere's circuital law
- (b) Gauss's law of electrostatic
- (c) Faraday's law of electromagnetic induction
- (d) Gauss's law of magnetostatics

ANS: C

Q. 4) The equivalent circuit of a zener diode consists of

- (a) A resistance in parallel with DC battery
- (b) A capacitance in series with DC battery
- (c) A capacitance in series with current source
- (d) 'A small dynamic resistance in series with DC battery'

ANS: D

Zener diode:

- A Zener diode is a semiconductor device that allows **current to flow either in a forward or reverse direction**.
- Since it is **highly doped**, the depletion layer is very thin and has a high voltage gradient and electric field.

Q. 5) Main advantage of fiber optic cable over co-axial cable is


- (a) Easy handling
- (b) Less weight
- (c) Easy testing
- (d) Low loss

ANS: D

The advantages of optical fibers are:

- Optical fibers have greater information-carrying capacity due to large bandwidth
- Optical fibers are free from electromagnetic interference and offer high signal security
- Optical fibers suffer less attenuation than coaxial cable and twisted wire cables.

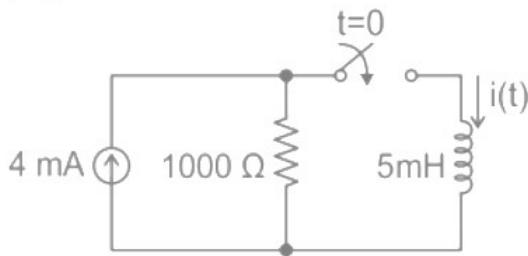Q. 6) Find the inductor current after the switch closes in the circuit.



(a) $i(t) = 4 \left(1 + e^{-\frac{t}{5}}\right)$ mA, and t is in μs

(b)

$$i(t) = 4 \left(1 + e^{\frac{t}{5}}\right)$$
 mA, and t is in μs

(c) $i(t) = 4 \left(1 - e^{-\frac{t}{5}}\right)$ mA, and t is in μs

(d) $i(t) = 4 \left(1 - e^{\frac{t}{5}}\right)$ mA, and t is in μs

ANS: C

$$\text{Time constant, } \tau = \frac{5 \times 10^{-3}}{1000} = 5 \times 10^{-6} \text{ sec}$$

At $t = 0$ or initial condition, the switch is open. So, the inductor circuit is open.


Hence inductor current is zero i.e. $i(0) = 0$

$$i(\infty) = 4 \text{ A}$$

Now the current equation is,

$$i(t) = 4 \left(1 - e^{-\frac{t}{5}}\right) \text{ mA and t is in } \mu s$$

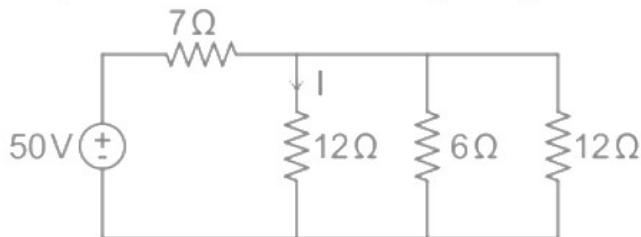Q. 7) Calculate the current 'I' flowing through $12\ \Omega$ resistor in the circuit shown.



(a) 3.25 A

(b) 7.25 A

(c) 1.25 A

(d) 5.55 A

ANS: C

$$\text{By applying KVL, } \frac{V-50}{7} + \frac{V}{12} + \frac{V}{6} + \frac{V}{12} = 0$$

$$\therefore V = 15\text{ V.}$$

$$\text{The current passes through } 12\ \Omega = \frac{15}{12} = 1.25\text{ A}$$

Q. 8) The phase constant of a good dielectric with $\epsilon_r = 1.5$ and $\mu_r = 6$ at 200 MHz is:

(a) $\pi\text{ rad/s}$

(b) $4\pi\text{ rad/s}$

(c) $2\pi\text{ rad/s}$

(d) $1.5\pi\text{ rad/s}$

ANS: B

Given:

$$\epsilon_r = 1.5$$

$$\mu_r = 6$$

$$f = 200 \text{ MHz}$$

$$\beta = \omega \sqrt{\mu \epsilon}$$

$$\beta = 2\pi f \sqrt{\mu_r \mu_0 \epsilon_r \epsilon_0}$$

$$\therefore c = \frac{1}{\sqrt{\epsilon_0 \mu_0}} = 3 \times 10^8 \text{ m/s}$$

On solving we'll get:

$$\beta = 4\pi$$

Q. 9) Hall effect can be used to measure

1. Carrier concentration
2. Type of semiconductor
3. Magnetic field
4. Conductivity

(a) 1 only

(b) 1 and 3 only

(c) 1, 2 and 4 only

(d) All of the above

ANS: C


Q. 10) A good transimpedance amplifier has

- (a) low input impedance and high output impedance.
- (b) high input impedance and high output impedance.
- (c) high input impedance and low output impedance.
- (d) low input impedance and low output impedance.

ANS: D

Type of Amplifier	R_{in}	R_{out}
Voltage Amplifier	High	Low
Current Amplifier	Low	High
Transconductance	High	High
Transimpedance amplifier	Low	Low

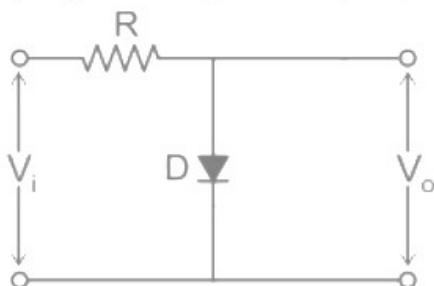
Q. 11) Following circuit is _____ clipper.



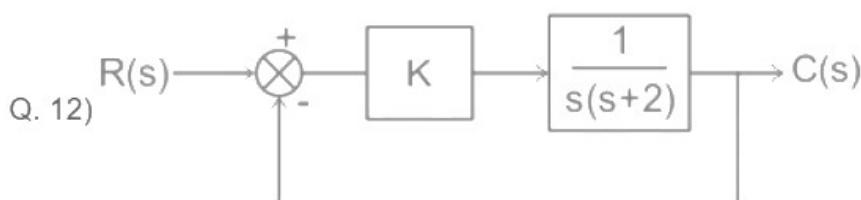- (a) Shunt negative
- (b) Series negative
- (c) Shunt positive
- (d) Series positive

ANS: C

The circuit clips the positive half of the input and the diode is connected in parallel to the load, therefore the circuit is said to be Shunt positive clipper.



For $r(t) = 0.9 t$, it is required that the steady state error should be less than 0.05. The value of gain K of proportional controller for the system shown above is _____.
 _____.

- (a) $K > 40$
- (b) $K > 36$
- (c) $K < 36$
- (d) $K < 40$

ANS: B

From the block diagram,

$$G(s) H(s) = \frac{K}{s(s+2)}$$

$$K_v = \lim_{s \rightarrow 0} s \cdot \frac{K}{s(s+2)}$$

$$= \lim_{s \rightarrow 0} \frac{K}{(s+2)} = \frac{K}{2}$$

$$e_{ss} < 0.05$$

$$\Rightarrow \frac{A}{K_v} < 0.05$$

$$\Rightarrow \frac{0.9}{\left(\frac{K}{2}\right)} < 0.05$$

$$\Rightarrow \frac{2(0.9)}{K} < 0.05$$

$$\Rightarrow K > \frac{1.8}{0.05}$$

$$\Rightarrow K > 36$$

Q. 13) 2's complement of -7 is

(a) 0111

(b) 1000

(c) 1111

(d) 1001

ANS: D

The binary form of 7 \leftrightarrow 0111

1's complement of -7 = 1(for sign) (000)(1's complement of 7)

$$= 1000$$

2's complement of -7 = 1's complement + 1 = 1000 + 1 = 1001

Q. 14) Given $(125)_R = (203)_5$. The value of radix R will be

(a) 26

(b) 10

(c) 8

(d) 6

ANS: D

$$(125)_R = (203)_5$$

If the two numbers are equivalent, they will remain equal in other number systems as well.

Converting both the sides to decimal and equating, we get:

$$1 \times R^2 + 2 \times R^1 + 5 \times R^0 = 2 \times 5^2 + 0 \times 5^1 + 3 \times 5^0$$

$$R^2 + 2R + 5 = 50 + 3$$

$$R^2 + 2R - 48 = 0$$

$$R^2 + 8R - 6R - 48 = 0$$

$$R(R + 8) - 6(R + 8) = 0$$

$$(R + 8)(R - 6) = 0$$

The valid value of R = 6

Q. 15) The Q-factor of an RLC circuit is 5 at its resonance frequency of 2 kHz. Find the bandwidth of the circuit.

(a) 10 kHz

(b) 400 Hz

(c) 1 kHz

(d) 200 Hz

ANS: B

We know that Quality factor (Q) is the ratio of resonance frequency and bandwidth, i.e.,

$$Q = \frac{f_o}{B.W}$$

$$\Rightarrow B.W = \frac{f_o}{Q}$$

$$B.W = \frac{2000}{5}$$

$$= 400 \text{ Hz}$$

Q. 16) What is the peak reverse voltage of a diode?

(a) The maximum amount of voltage the diode can withstand in Forward-bias

(b) The maximum amount of voltage the diode can withstand in reverse-bias

(c) The forward voltage drop of a diode

(d) The internal voltage drop of a diode

ANS: B

Q. 17) The break away point in the root loci plot for the loop transfer function $G(S) = \frac{K}{S(S+3)^2}$ is

(a) -2.5

(b) -1.0

(c) -2.0

(d) -0.5

ANS: B

Given loop transfer function is, $G(s) = \frac{K}{s(s+3)^2}$

For breakaway points, $\frac{dK}{ds} = 0$

$$\Rightarrow \frac{d}{ds} [s(s+3)^2] = 0$$

$$\Rightarrow \frac{d}{ds} [s^3 + 6s^2 + 9s] = 0$$

$$\Rightarrow 3s^2 + 12s + 9 = 0$$

$$\Rightarrow s^2 + 4s + 3 = 0$$

$$\Rightarrow (s + 3)(s + 1) = 0$$

$$\Rightarrow s = -3, s = -1$$

$s = -1$ is a valid breakaway point.

Q. 18) A 400 W carrier is amplitude modulated and has side-band power of 50 W. The depth of modulation is

(a) 1

(b) 0.45

(c) 0.50

(d) 0.55

ANS: C

In Amplitude modulated system

Power in side band is given by

$$P_{SB} = P_c \left(\frac{\mu^2}{2} \right)$$

Hence

$$\frac{P_{SB}}{P_c} = \left(\frac{\mu^2}{2} \right)$$

$$\frac{50}{400} = \left(\frac{\mu^2}{2} \right)$$

$$\mu = 0.5$$

Q. 19) A transmission line of surge impedance 300Ω is connected to a load of 300Ω . The reflection coefficient of transmission line at the load end will be

(a) 0

(b) -1

(c) 2

(d) +1

ANS: A

Given that,

Surge impedance of transmission line $Z_C = 300 \Omega$

Load impedance at the end transmission line $Z_L = 300 \Omega$

Therefore, reflection coefficient of transmission line at load end is

$$\tau_r = \frac{300 - 300}{300 + 300} = 0$$

Q. 20) Find the position constant and steady-state error, respectively, for an open-loop transfer function given by.

$$H(s)G(s) = \frac{(s+3)}{(s+1)(s+2)}$$

(a) 2, 0.8

(b) 11, 9

(c) 1.5, 0.4

(d) 2, 0.5

ANS: C

$$H(s)G(s) = \frac{(s+3)}{(s+1)(s+2)}$$

We have to determine the position error constant (K_p),

$$K_p = \text{position error constant} = \lim_{s \rightarrow 0} G(s) H(s)$$

$$\lim_{s \rightarrow 0} G(s) H(s) = \frac{(s+3)}{(s+1)(s+2)}$$

$$K_p = \frac{3}{2} = 1.5$$

Now the steady-state error would be:

$$Error = \frac{1}{1+K_p}$$

$$Error = \frac{1}{1+1.5} = 0.4$$

Q. 21) Consider the following statement:

Fourier Series of any periodic function $x(t)$ can be obtained if,

$$1. \int_{t_1}^{\infty} |x(t)| < \infty$$

2. Signal $x(t)$ must have a finite number of maxima and minima in the expansion interval.

3. $x(t)$ can have an infinite number of finite discontinuities in the expansion interval.

4. $x^2(t)$ is absolute summable

Which of the statement is/are false:

(a) 1 and 4

(b) 1 and 2

(c) 3 only

(d) 1 and 3

ANS: C

Q. 22) Kirchhoff's current law is based upon which of the following fact?

(a) Charge accumulation is possible at node.

(b) There is a possibility for a node to store energy.

(c) Charge accumulation may or may not be possible.

(d) There cannot be an accumulation of charge at a node.

ANS: D

Q. 23) In phase modulation, phase deviation is proportional to:

- (a) Carrier phase
- (b) Message signal
- (c) Carrier amplitude
- (d) Message signal frequencies

ANS: B

A general expression for a phase-modulated wave is:

$$x_{PM}(t) = A \cos [2\pi f_c t + k_p m(t)]$$

The instantaneous angle is given as:

$$\phi_i(t) = 2\pi f_c t + k_p m(t)$$

Phase deviation is, therefore:

$$\Delta[\phi_i(t)] = k_p m(t)$$

Conclusion: The phase deviation is proportional to the message signal.

Q. 24) In a bipolar junction transistor, the emitter efficiency is (p-n-p transistor):

- (a) $\frac{\text{Current of injected carriers at } J_E}{\text{total collector current}}$
- (b) $\frac{\text{Current of injected carriers at } J_E}{\text{total emitter current}}$
- (c) $\frac{\text{Current of injected carriers at } J_C}{\text{total collector current}}$
- (d) $\frac{\text{Current of injected carriers at } J_C}{\text{total emitter current}}$

ANS: B

Q. 25) In an open device, current through it is

- (a) zero and voltage is unknown.
- (b) known and voltage is zero.
- (c) zero and voltage is also zero.
- (d) unknown and voltage is also unknown.

ANS: A

Q. 26) A diode for which you can change the reverse bias and thus vary the capacitance is called a -

- (a) Switching diode
- (b) Varactor diode
- (c) Tunnel diode
- (d) Zener diode

ANS: B

Varactor diode refers to the variable Capacitor diode, which means the capacitance of the diode varies linearly with the applied voltage when it is **reversed biased**.

Q. 27) A wave is incident from free-space onto a dielectric region of dielectric constant $\epsilon_r = 4$, The wave impedance in the dielectric is:

(a) 55.5Ω

(b) 100.5Ω

(c) 108.6Ω

(d) 188.5Ω

ANS: D

The wave impedance is given by the expression:

$$\eta = \eta_0 \sqrt{\frac{\mu_r}{\epsilon_r}}$$

η_0 is the intrinsic impedance of free space = 377Ω

Calculation:

$$\epsilon_r = 4, \mu_r = 1$$

$$\eta = 377 \sqrt{\frac{1}{4}}$$

$$= 188.5 \Omega$$

Q. 28) An LTI system will be stable, if the impulse response $h(t)$ has the restriction

(a) $\int_{-\infty}^{\infty} |h(\tau)| d\tau < \infty$

(b) $\int_{-\infty}^{\infty} h(\tau) \cdot h(t - \tau) d\tau = 0$

(c) $y(t) = h(t) \cdot x(t)$

(d) $h(0) = 0$

ANS: A

Q. 29) If N is the doping level of substrate and V is the effective voltage across the junction in a MOSFET, then the depletion region width for the junction is given by:

(a) $\sqrt{\frac{2\epsilon_{st}\epsilon_0 V}{qN}}$

(b) $\sqrt{\frac{2\epsilon_{st}\epsilon_0 qV}{N}}$

(c) $\sqrt{\frac{2\epsilon_{st}N}{qV}}$

(d) $\frac{2\epsilon_{st}\epsilon_0 V}{qN}$

ANS: A

The Depletion region width of MOSFET is given by:

$$W = \sqrt{\frac{2\epsilon_{si}\epsilon_0 V}{qN}}$$


Where v is applied potential

q = electron charge

N =Doping Concentration

ϵ is the permittivity of materials

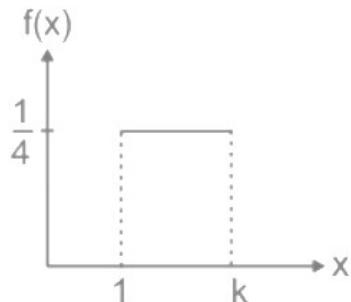Q. 30) The continuous random variable X has pdf $f(x)$ as shown below. Find the variance.



(a) $\frac{2}{\sqrt{3}}$

(b) $\frac{4}{3}$

(c) $\frac{16}{9}$

(d) $\frac{5}{3}$

ANS: B

The area under the curve must be 1,

$$\Rightarrow \frac{1}{4}(k - 1) = 1$$

$$\Rightarrow k = 5$$

$$\text{Variance} = \frac{(b-a)^2}{12} = \frac{(5-1)^2}{12} = \frac{16}{12} = \frac{4}{3}$$

Q. 31) Which of the following will not be present in the trigonometric Fourier series of an even function of time?

- (a) sine term
- (b) cosine term
- (c) DC term
- (d) odd harmonic term

ANS: A

Symmetry	Condition	Fourier series
Even	$f(t) = f(-t)$	The DC and cosine terms can exist
Odd	$f(t) = -f(-t)$	Sine terms can exist
Half wave	$f(t \pm T/2) = -f(t)$	Odd harmonics
	$f(t \pm T/2) = f(t)$	Even harmonics

Q. 32) A source produces three symbols A, B and C with probabilities, $P(A) = \frac{1}{2}$, $P(B) = \frac{1}{4}$ and $P(C) = \frac{1}{4}$. The source entropy is

- (a) $\frac{1}{2}$ bit/symbol
- (b) 1 bit/symbol
- (c) $1 \frac{1}{4}$ bits/symbol
- (d) $1 \frac{1}{2}$ bits/symbol

ANS: D

Given:

$$P(A) = \frac{1}{2}, P(B) = \frac{1}{4} \text{ and } P(C) = \frac{1}{4}$$

The entropy will be:

$$H = \frac{1}{2} \log_2 (2) + \frac{1}{4} \log_2 4 + \frac{1}{4} \log_2 4$$

$$H = \frac{1}{2} + \frac{2}{4} + \frac{2}{4}$$

$$H = 6/4 = 1 \frac{1}{2} \text{ bits/symbol}$$

Q. 33) What is the effect of current shunt feedback in an amplifier?

- (a) Decrease the input resistance and increase the output resistance
- (b) Decrease both the input and output resistances
- (c) Increase the input resistance and decrease the output resistance
- (d) Increase both input and output resistances

ANS: A

Q. 34) For which of the following calculations can superposition principle be applied?

- (a) Voltage and power
- (b) Current and power
- (c) Voltage, current and power
- (d) Voltage and current

ANS: D

Q. 35) Consider a signal $x(t) = 4 \cos(2t/3) + 8 \sin(0.5t) + 7 \sin(t/3 - \pi/6)$ Calculate the fundamental period.

- (a) 6π seconds
- (b) 2π seconds
- (c) 12π seconds
- (d) π seconds

ANS: C

Given:

$$x(t) = 4 \cos\left(\frac{2t}{3}\right) + 8 \sin(0.5t) + 7 \sin\left(\frac{t}{3} - \frac{\pi}{6}\right)$$

$$T_1 = \frac{\frac{2\pi}{2}}{3} = 3\pi$$

$$T_2 = \frac{2\pi}{0.5} = 4\pi$$

$$T_3 = \frac{2\pi}{\frac{1}{3}} = 6\pi$$

Time period = L.C.M. (T_1, T_2, T_3)

$$= \text{L.C.M.}(3\pi, 4\pi, 6\pi)$$

$$= 12\pi$$

Q. 36) The characteristic impedance of an 80 cm long lossless transmission line having $L = 0.25 \mu\text{H/m}$ and $C = 100 \text{ pF/m}$ will be

(a) 25Ω

(b) 40Ω

(c) 50Ω

(d) 80Ω

ANS: C

$$Z_0 = \sqrt{\frac{L}{C}}$$

Calculation:


With $L = 0.25 \mu\text{H}/\text{m}$ and $C = 100 \text{ pF}/\text{m}$, we get:

$$Z_0 = \sqrt{\frac{0.25 \times 10^{-6}}{100 \times 10^{-12}}}$$

$$Z_0 = \sqrt{2500}$$

$$Z_0 = 50 \Omega$$

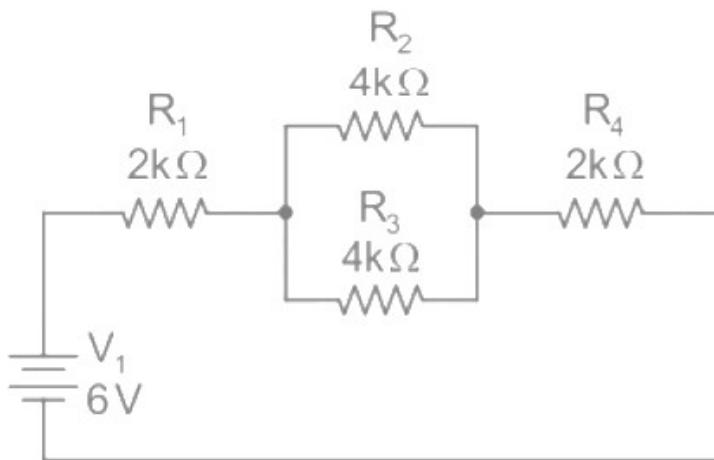Q. 37) What is the total current (mA) in the given circuit?



- (a) 1 mA
- (b) 1.6 mA
- (c) 0.75 mA
- (d) 0.5 mA

ANS: A

The equivalent resistance of the parallel combination of R_2 and R_3 will be:

$$R_{eq} = \frac{4k \times 4k}{4k + 4k} = 2k\Omega$$

The equivalent resistance will be the series combination of $2\text{ k}\Omega + 2\text{ k}\Omega + 2\text{ k}\Omega$, i.e.

$$R'_{eq} = 6\text{ k}\Omega$$

The current flowing across the circuit will be:

$$I = \frac{6}{6k} = 1\text{ mA}$$

Q. 38) Which of the following gates is required to build a half adder?

- (a) EX-OR gate and OR gate
- (b) EX-OR gate and NOR gate
- (c) Four NAND gate
- (d) EX-OR gate and AND gate

ANS: D

Q. 39) Which one of the following is not a basic MOSFET device type?

- (a) Enhancement P-channel MOSFET
- (b) Depletion N-channel MOSFET
- (c) Narrow P-channel MOSFET
- (d) Enhancement N-channel MOSFET

ANS: C

Q. 40) The solution to the ordinary differential equation $\frac{d^2y}{dx^2} + \frac{dy}{dx} - 6y = 0$ is

(a) $y = c_1 e^{3x} + c_2 e^{-2x}$

(b) $y = c_1 e^{3x} + c_2 e^{2x}$

(c) $y = c_1 e^{-3x} + c_2 e^{2x}$

(d) $y = c_1 e^{-3x} + c_2 e^{-2x}$

ANS: C

The given ordinary differential equation (ODE) is

$$\frac{d^2y}{dx^2} + \frac{dy}{dx} - 6y = 0$$

The given equation can be written as

$$D = d/dx$$

$$(D^2 + D - 6)y = 0$$

The auxiliary equation is $D^2 + D - 6 = 0 \Rightarrow (D - 2) \times (D + 3) = 0$

The roots of auxiliary equation are -3 and 2

The complementary function C.F = $c_1 e^{-3x} + c_2 e^{2x}$

Since the RHS = 0, **there is no particular integral**

The solution is $y = c_1 e^{-3x} + c_2 e^{2x}$

Q. 41) The depletion region in a Junction Diode contains

- (a) only charge carriers (of minority type and majority type)
- (b) no charge at all
- (c) vacuum and no atoms at all
- (d) only ions, i.e., immobile charges

ANS: D

Q. 42) Which of the following is responsible for thermal runaway in BJT?

- (a) Change in β value with temperature
- (b) Increase in forward bias current
- (c) Increase in junction voltage
- (d) Increase in reverse biased minority current.

ANS: D

Q. 43) In a non-inverting OPAMP, if $R_1 = 20$ K ohms and $R_f = 200$ K ohms, then find the gain of the amplifier.

(a) 11

(b) 10

(c) 1.1

(d) 100

ANS: A

$$R_1 = 20 \text{ k}\Omega \text{ and } R_2 = 200 \text{ k}\Omega$$

The voltage gain

$$A_v = 1 + \frac{R_2}{R_1}$$

$$A_v = 1 + \frac{200}{20}$$

$$= 11$$

Q. 44) Figure 1 represents a Y network of three equal resistances of $5\ \Omega$ each. The equivalent delta network of figure 2 will comprise of three equal resistances each equal to:

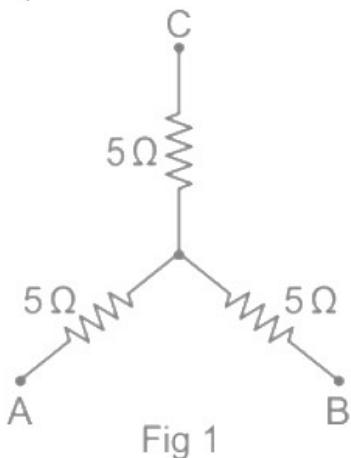


Fig 1

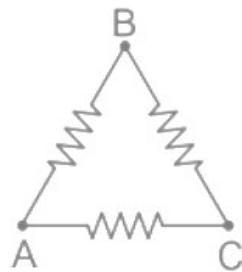


Fig 2

- (a) $15\ \Omega$
- (b) $2.5\ \Omega$
- (c) $5\ \Omega$
- (d) $10\ \Omega$

ANS: A

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Calculation:

Given $R_1 = 5 \Omega$, $R_2 = 5 \Omega$, $R_3 = 5 \Omega$

$$R_a = \frac{5 \times 5 + 5 \times 5 + 5 \times 5}{5}$$

$$R_a = 15 \Omega$$

Similarly,

$$R_b = 15 \Omega$$

$$R_c = 15 \Omega$$

Q. 45) Impedance of an inductor is twice that of a capacitor at a particular frequency f . If they are connected in series, what is the resonant frequency?

(a) $\frac{f}{\sqrt{2}}$

(b) $\sqrt{2}f$

(c) $2f$

(d) $4f$

ANS: B

When impedance of an inductor is twice that of a capacitor and they are connected in series, their resonant frequency is given by:

$$X_L = 2X_C$$

$$\omega L = \frac{2}{\omega C}$$

$$\omega^2 = \frac{2}{LC}$$

$$\omega = \frac{\sqrt{2}}{\sqrt{LC}}$$

$$2\pi f_{\text{new}} = \frac{\sqrt{2}}{\sqrt{LC}}$$

$$f_{\text{new}} = \frac{\sqrt{2}}{2\pi\sqrt{LC}}$$

Since, resonant frequency (f) = $\frac{1}{2\pi\sqrt{LC}}$

$$f_{\text{new}} = \sqrt{2} f$$

Q. 46) The main purpose of modulation is to

- (a) Combine two waves of different frequencies
- (b) Achieve wave shaping of the carrier wave
- (c) Transmitting low frequency information over long distance efficiently
- (d) Produce side bands

ANS: C

Q. 47) $H(e^{j\omega})$ is the frequency response of a discrete time LTI system and $H_1(e^{j\omega})$ is the frequency response of its inverse function. Then

- (a) $H(e^{j\omega})H_1(e^{j\omega}) = 1$
- (b) $H(e^{j\omega})H_1(e^{j\omega}) = \delta(\omega)$
- (c) $H(e^{j\omega}) * H_1(e^{j\omega}) = 1$
- (d) $H(e^{j\omega}) * H_1(e^{j\omega}) = \delta(\omega)$

ANS: A

D.T.F.T

Discrete-time Fourier transform is defined by

$$H(e^{j\omega}) = \sum_{n=-\infty}^{\infty} h[n] e^{-j\omega n}$$

Inverse function of $x(n)$ is defined as:

$$h_1(n) = 1/h(n)$$

$$H_1(e^{j\omega}) = 1/H(e^{j\omega})$$

$$H(e^{j\omega}) H_1(e^{j\omega}) = 1$$

Q. 48) The bandwidth of a single stage amplifier is _____ that of a multistage amplifier

- (a) More than
- (b) The same as
- (c) Less than
- (d) Data insufficient

ANS: A

- The gain of the multistage amplifier increases.
- As the product of gain and bandwidth is constant, **the bandwidth decreases**. Hence the bandwidth of a single-stage amplifier is **more than** that of a multistage amplifier

Q. 49) For satellite communication the standard uplink and downlink frequencies, respectively, in C-band are:

- (a) 6 GHz and 4 GHz
- (b) 12 GHz and 8 GHz
- (c) 4 GHz and 6 GHz
- (d) 12 GHz and 9 GHz

ANS: A

Q. 50) Convert hex number to decimal.

$(0101)_{16}$

(a) 572

(b) 527

(c) 257

(d) 253

ANS: C

Given,

Hexadecimal number is $(0101)_{16}$

Expanding according to equation 1,

$$\begin{aligned} & (0 \times 16^3) + (1 \times 16^2) + (0 \times 16^1) + (1 \times 16^0) \\ &= (0 \times 4096) + (1 \times 256) + (0 \times 16) + (1 \times 1) \\ &= (257)_{10} \end{aligned}$$

So, the decimal equivalent of the given hexadecimal number is $(257)_{10}$

Q. 51) A 120 Ah capacity battery can deliver a current of 8 A for a period of

(a) 20 hrs

(b) 15 hrs

(c) 12 hrs

(d) 8 hrs

ANS: B

Given that,

capacity of battery = 120 AH

current = 8A

Now backup time can be calculated as

Backup time = 120/8

Backup time = 15 hours

A 120 Ah capacity battery can deliver a current of 8A for a period of **15 hours**

Q. 52) A capacitor of capacitance 50 micro farads is charged to a potential difference of 200 Volts. Find out energy stored in the condenser ?

- (a) 1 joule
- (b) 100 milli joule
- (c) 10 milli joule
- (d) 100 joule

ANS: A

Given:

$$C = 50 \mu\text{F}, V = 200\text{V}$$

The energy stored in the capacitor is:

$$U = \frac{1}{2} CV^2$$

$$U = \frac{1}{2} (50 \times 10^{-6}) \times (200)^2$$

$$U = 1\text{J}$$

Q. 53) The formula for determining resonant frequency (f_r) of series RLC Circuit is

(a) $f_r = \sqrt{LC}$

(b) $f_r = \frac{1}{\sqrt{LC}}$

(c) $f_r = 2\pi\sqrt{LC}$

(d) $f_r = \frac{1}{2\pi\sqrt{LC}}$

ANS: D

Q. 54) In a certain series resonant circuit $V_c = 100$ V, $V_L = 100$ V and $V_R = 35$ V. The source voltage is

(a) 100 V

(b) 135 V

(c) 65 V

(d) 35 V

ANS: D

Given:

$$V_C = 100 \text{ V}, V_L = 100 \text{ V} \text{ and } V_R = 35 \text{ V}$$

At resonance, the source voltage will be equal to the voltage across the resistor, i.e.

$$V_S = V_R = 35 \text{ V}$$

Q. 55) During forward bias and reverse bias, an ideal diode has _____ respectively.

- (a) zero conductance & zero resistance
- (b) zero conductance & infinite resistance
- (c) infinite conductance & infinite resistance
- (d) infinite conductance & zero resistance

ANS: C

Q. 56) If the carrier modulated by a digital bit stream had one of the possible phases of 0° , 90° , 180° and 270° then the modulation is called

- (a) BPSK
- (b) QPSK
- (c) QAM
- (d) MSK

ANS: B

Q. 57) Which one of the following is an element which samples the continuous signal into sequence pulses appearing at regular interval of time?

- (a) Coupler
- (b) Sampler
- (c) A/D Converter
- (d) D/A Converter

ANS: B

Q. 58) The 8085 Microprocessor has

- (a) 8 - bit data bus 16 - bit address bus
- (b) 8 - bit data bus 8 - bit address bus
- (c) 16 - bit data bus 8 - bit address bus
- (d) 16 - bit data bus 16 - bit address bus

ANS: A

Q. 59) In TTL family, the Totem-pole circuit on the output is used to provide

_____.

- (a) active pull up and active pull down
- (b) active pull up
- (c) active pull down
- (d) inactive output state

ANS: A

Q. 60) The unit impulse response of a system is $h(t) = e^{-t}$, $t \geq 0$. For this system, the steady state value of the output for unit step input is equal to

- (a) -1
- (b) 0
- (c) 1
- (d) ∞

ANS: C

Q. 61) Find out the equivalent of $A + A' + B'$.

(a) 1

(b) AB

(c) A

(d) B

ANS: A

$$Y = A + A' + B'$$

By using Inverse law

$$Y = 1 + B'$$

$$Y = 1$$

Q. 62) The values of c for which the function $f(x)$ is a p.d.f. is?

$$f(x) = \begin{cases} \frac{c}{\sqrt{x}}, & 0 < x < 4 \\ 0, & otherwise \end{cases}$$

(a) $\frac{1}{2}$

(b) $\frac{1}{3}$

(c) $\frac{1}{4}$

(d) $\frac{1}{6}$

ANS: C

$$\text{PDF } = f(x) = \begin{cases} \frac{c}{\sqrt{x}}, & 0 < x < 4 \\ 0, & otherwise \end{cases}$$

Using Equation (2):

$$\int_0^4 \frac{c}{\sqrt{x}} dx = 1$$

$$[2c\sqrt{x}]_0^4 = 1$$

$$4c = 1$$

$$c = \frac{1}{4}$$

Q. 63) The probability of having an electron in the Fermi level for semiconductor is:

- (a) 1
- (b) infinity
- (c) 0.5
- (d) Cannot be defined if the temperature is not given

ANS: C

For metal, the probability is 1.

For semiconductors, the probability is 0.5.

For insulators, the probability is 0.

Q. 64) Negative feedback in amplifier:

- (a) Increase stability
- (b) Increases noise
- (c) Increases frequency distortion
- (d) Increases gain

ANS: A

The negative feedback in amplifiers causes:

- Reduced the gain and **increases the stability**.
- Increases the bandwidth to maintain constant gain-bandwidth product
- Reduces the distortion and noise in the amplifier
- The signal-to-noise ratio is not affected.

Q. 65) The battery with a 1400 mAh can supply 2.8 Ampere current for:

- (a) 60 minutes
- (b) 30 minutes
- (c) 100 minutes
- (d) 50 minutes

ANS: B

The capacity of battery = 1400 mAh

Current delivered = 2.8 A

Duration of time (T) will now be:

$$T = \frac{1400 \text{ mAh}}{2.8 \text{ A}}$$

$$T = \frac{1400 \times 10^{-3} \text{ h}}{2.8 \text{ A}}$$

$$T = 0.5 \text{ hr} = 0.5 \times 60 \text{ min}$$

$$T = 30 \text{ mins}$$

Q. 66) In an impedance smith chart a clockwise movement along a constant resistance circle gives rise to

- (a) a decrease in value of reactance
- (b) a increase in value of reactance
- (c) No change in value of reactance
- (d) No change in value of impedance

ANS: B

Q. 67) The binary equivalent of the octal number 456 is _____.

- (a) 100111101
- (b) 100101110
- (c) 101011110
- (d) 101001101

ANS: B

- From the above table, the binary equivalent of 6 is 110.
- The binary equivalent of 5 is 101.
- The binary equivalent of 4 is 100.

Hence, the binary equivalent of the octal number 456 is 100101110

Q. 68) Class C amplifiers are used as

- (a) RF amplifiers
- (b) AF amplifiers
- (c) Small signal amplifiers
- (d) IF amplifiers

ANS: A

Power Amplifier	Conduction Angle	Maximum Efficiency	Figure of Merit
Class A	360°	50%	2
Class B	180°	78.5%	0.4
Class AB	180° - 360°	50 - 78.5%	0.4 - 2
Class C	< 180°	≥ 90°	< 0.25

Q. 69) Power amplifiers generally use transformer coupling because transformer coupling provides

- (a) Cooling of the circuit
- (b) Distortion less output
- (c) Good frequency response
- (d) Impedance matching

ANS: D

Advantages of transformer coupling:

- **An excellent impedance matching is provided.**
- The gain achieved is higher.
- There will be no power loss in the collector and base resistors.
- Efficient in operation.

Q. 70) The directivity of an antenna array can be increased by adding more antenna elements, as a larger number of elements:

- (a) improves the radiation efficiency
- (b) increases the effective area of the antenna
- (c) results in a better impedance matching
- (d) allows more power to be transmitted by the antenna

ANS: B

Effective Area (A_c):

It describes how much power the antenna can capture from a given plane wave.

$A_c = \frac{\lambda^2}{4\pi} D$ From the above, it is clear that if G_d increases then D also increases. This indicates that A_c also increases.

Q. 71) A proportional plus derivative controller:

1. has high sensitivity.
2. increases the stability of the system.
3. improves steady-state accuracy.

Which of the above statements are correct?

(a) 1, 2, and 3

(b) 1 and 2 only

(c) 1 and 3 only

(d) 2 and 3 only

ANS: B

Q. 72) The result of $h(2t) * \delta(t - t_0)$ (" * " denotes convolution and " $\delta()$ " denotes the Dirac delta function) is:

(a) $h(2t - 2t_0)$

(b) $h(2t_0 - 2t)$

(c) $h(-2t - 2t_0)$

(d) $h(2t + 2t_0)$

ANS: A

Given signal is $h(2t)$ and convolution is done with $\delta(t - t_0)$

$$h(2t) * \delta(t - t_0) = h(2(t - t_0))$$

$$h(2t) * \delta(t - t_0) = h(2t - 2t_0)$$

Q. 73) A capacitor carries a charge of 0.1 C at 5.0 V. Its capacitance is

(a) 0.05 F

(b) 0.02 F

(c) 0.5 F

(d) 0.2 F

ANS: B

Given:

$$Q = 0.1 \text{ C}, V = 5.0 \text{ V}$$

From equation (1);

$$C = \frac{0.1}{5}$$

$$C = 0.02 \text{ F}$$

Q. 74) The 555 timer can be used in which of the following configurations?

- (a) astable, monostable and bistable
- (b) monostable, toggled
- (c) astable, toggled
- (d) bistable, tristable

ANS: A

Q. 75) An unit impulse function in continuous form is defined to be

(a) $\delta(t) = t$

(b) $\delta(t) = 1$

(c) $\delta(t) = \begin{cases} \infty, & t = 0 \\ 0, & t \neq 0 \end{cases}$

(d) $\delta(t) = \begin{cases} 0, & t = 0 \\ 1, & t \neq 0 \end{cases}$

ANS: C

Q. 76) Consider the analog signal $x(t) = 3 \cos 100 \pi t$. If the signal is sampled at 200 Hz, the discrete time signal obtained will be

(a) $3 \cos(\pi n/4)$

(b) $3 \cos(\pi n/2)$

(c) $3 \cos(\pi n)$

(d) $3 \cos(\pi n/3)$

ANS: B

For a signal $x(t)$ sampled with a sampling interval T_s , the discrete sequence can be written as:

$$x(n) = x(t)|_{t=nT_s}$$

T_s = sampling interval

Analysis:

$$x(t) = 3 \cos 100\pi t$$

$$f_s = 200 \text{ Hz}, T_s = 1/200 = 0.005 \text{ sec}$$

$$x(n) = 3 \cos 100\pi(n/200)$$

$$x(n) = 3 \cos (\pi n/2)$$

Q. 77) A capacitor is charged through a resistance R then the time constant of the circuit is

(a) $\frac{R}{C}$

(b) $\frac{1}{RC}$

(c) RC

(d) $\frac{C}{R}$

ANS: C

Q. 78) A uniform plane wave in the free space is normally incident on an infinitely thick dielectric slab (dielectric constant $\epsilon_r = 9$). The magnitude of the reflection coefficient is

(a) 0

(b) 0.3

(c) 0.5

(d) 0.8

ANS: C

The magnitude of the reflection coefficient = $|\Gamma|$

$$\Gamma = \frac{\sqrt{\epsilon_{r1}} - \sqrt{\epsilon_{r2}}}{\sqrt{\epsilon_{r1}} + \sqrt{\epsilon_{r2}}}$$

Calculation:

$$\Gamma = \frac{1-3}{1+3} = -0.5$$

$$|\Gamma| = 0.5$$

Q. 79) Built-in potential V_0 of a junction depends on:

(a) Doping densities and Temperature

(b) Only Temperature

(c) Cross sectional area of the junction

(d) Doping densities only

ANS: A

Q. 80) Which of the following is correct for a D-type flip-flop ?

- (a) The Q output is either SET or RESET as soon as the D input goes HIGH or LOW
- (b) The output complement follows the input when enabled
- (c) Only one of the inputs can be HIGH at a time
- (d) The output toggles if one of the inputs is held HIGH

ANS: A

Q. 81) For a thermally grown silicon dioxide layer, in a MOSFET, the leakage current between the gate and channel is:

- (a) 0
- (b) Very small
- (c) Large
- (d) Very large

ANS: B

Q. 82) The r.m.s. value of an a.c. signal is 10V. It's peak value will be:

- (a) 6.37 V
- (b) 14.14 V
- (c) 141 V
- (d) None of these

ANS: B

RMS value of an AC signal (sine wave)

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Where,

V_m : Maximum value or Peak value

Calculation:

$$V_{rms} = 10 \text{ V}$$

$$V_m = 10\sqrt{2}$$

$$V_m = 14.14 \text{ V}$$

Q. 83) In which combination, Ammeter is connected with circuit:

- (a) Series
- (b) Sometime series, sometimes parallel
- (c) Parallel
- (d) None of these

ANS: A

Ammeter:

1. The electrical instrument which is used to measure the electric current in an electric circuit is called an ammeter.
2. An **Ammeter** is connected in the series combination because the **current remains constant in the series combination**.
3. This helps in getting an accurate reading from the instruments

Q. 84) If the minimum range is to be doubled in a radar, the peak power has to be increased by a factor of

- (a) 4
- (b) 8
- (c) 16
- (d) 32

ANS: C

We observe that, $R \propto (P_t)^{1/4}$

Now, to double the range R , P_t has to be increased by a factor of 16

Q. 85) The transconductance of a JFET is computed at constant V_{DS} by:

- (a) Ratio of change in I_d to change of V_{gs}
- (b) Ratio of change in V_{gs} to change of I_d
- (c) Product of change in V_{gs} to change of I_d
- (d) Ratio of change in V_{ds} to change of I_d

ANS: A

Q. 86) Which register pair of 8085 is used to store the memory address for memory-related instructions?

- (a) B, C registers
- (b) H, L registers
- (c) A, Flag register
- (d) D, E registers

ANS: B

Q. 87) Two rectangular waveguides have dimensions of 1 cm × 0.5 cm and 1 cm × 0.25 cm respectively. Their respective cutoff frequencies will be

- (a) 15 GHz and 30 GHz
- (b) 15 GHz and 15 GHz
- (c) 30 GHz and 30 GHz
- (d) 30 GHz and 15 GHz

ANS: B

The minimum cutoff frequency in a rectangular waveguide is for TE₁₀

$$i.e. f_{c(10)} = \frac{c}{2} \sqrt{\frac{m^2}{a^2}} = \frac{c}{2a}$$

The cut off frequency is given by:

$$f_c = \frac{c}{2a} = \frac{3 \times 10^8}{2 \times 1 \times 10^{-2}} = 15 \text{ GHz}$$

It will be the same for both since the cut-off frequency is only dependent on broadside length (a).

Q. 88) What is the maximum frequency of modulating signal in FM system, if it has 8 significant sidebands, and the maximum bandwidth is 32 kHz?

- (a) 4 kHz
- (b) 8 kHz
- (c) 16 kHz
- (d) 2 kHz

ANS: D

BW = 32 KHz

Given FM system has 8 sidebands (significant) i.e. 8 sidebands on the positive side of frequency & 8 sidebands on the negative side of the frequency

So, It has sidebands up to order '8'.

According to carson rule:

Significant sideband upto order of $(\beta + 1)$ has B.W

$$\text{BW} = (\beta + 1) 2f_m$$

So,

$$32 = 8 \times 2 f_m$$

$$f_m = 2 \text{ kHz}$$

Q. 89) If X and Y are random variables such that $E[2X + Y] = 0$ and $E[X + 2Y] = 33$, then $E[X] + E[Y] = \underline{\hspace{2cm}}$.

(a) 9

(b) 6

(c) 13

(d) 11

ANS: D

$$E[2X + Y] = 0$$

$$2E[X] + E[Y] = 0 \quad \text{----(1)}$$

$$E[X + 2Y] = 33$$

$$E[X] + 2E[Y] = 33 \quad \text{----(2)}$$

Adding (1) and (2)

$$3E[X] + 3E[Y] = 33$$

$$E[X] + E[Y] = 11$$

Q. 90) The central tapping of the transformer in centre tapped full wave rectifier is used:

- (a) To isolate the load from secondary winding
- (b) To step up the voltage of the transformer
- (c) To step down the voltage of the transformer
- (d) To make both the diodes to conduct during alternate half cycles

ANS: D

Q. 91) A signal of maximum frequency of 10 kHz is sampled at Nyquist rate. The time interval between two successive samples is

- (a) 50 μ s
- (b) 100 μ s
- (c) 500 μ s
- (d) 1000 μ s

ANS: A


$$f_m = 10 \text{ kHz}$$

$$f_s = 20 \text{ kHz}$$

$$T_s \leq \frac{1}{2 \times 10}$$

$$T_s = 50 \mu\text{s}$$

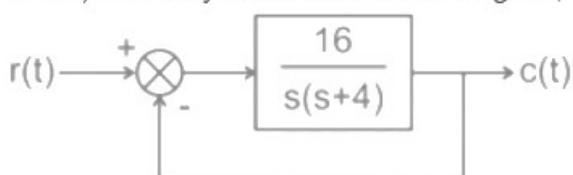Q. 92) In the system shown in the figure, $r(t) = \sin \omega t$



The steady-state response $c(t)$ will exhibit a resonance peak at a frequency of:

- (a) 4 rad/sec
- (b) $2\sqrt{2}$ rad/sec
- (c) 2 rad/sec
- (d) $\sqrt{2}$ rad/sec

ANS: B

The given feedback is a unity feedback system,

$$\begin{aligned} CLTF &= \frac{G(s)}{1+G(s)} = \frac{\frac{16}{s(s+4)}}{1+\frac{16}{s(s+4)}} \\ &= \frac{16}{s(s+4)+16} = \frac{16}{s^2+4s+16} \end{aligned}$$

The characteristic equation is given by;

$$s^2 + 4s + 16 = 0$$

Comparing this with the standard 2nd order characteristic equation $s^2 + 2\xi\omega_n s + \omega_n^2 = 0$, we see that,

$$\omega_n^2 = 16.$$

$$\text{So, } \omega_n = 4$$

$$\text{And, } 2\xi\omega_n = 4$$

$$\text{So, } \xi = 0.5 = \frac{1}{2}$$

So, the resonant frequency is given by;

$$\begin{aligned} \omega_r &= \omega_n \sqrt{1 - 2\xi^2} \\ \omega_r &= 4 \sqrt{1 - 2\left(\frac{1}{2}\right)^2} \\ &= 4 \sqrt{1 - \frac{1}{2}} = 2\sqrt{2} \text{ rad/sec} \end{aligned}$$

Q. 93) The term heterodyning refers to

- (a) Frequency conversion
- (b) Frequency mixing
- (c) Frequency conversion & mixing
- (d) None of the mentioned

ANS: C

Q. 94) For the open loop transfer function $G(s)H(s) = \frac{K}{s(s+4)(s+5)}$. The point of intersection of root locus with imaginary axis is _____.

- (a) $\pm j2\sqrt{5}$
- (b) $\pm j4\sqrt{5}$
- (c) $\pm j\sqrt{5}$
- (d) $\pm j3\sqrt{5}$

ANS: A

$$G(s)H(s) = \frac{K}{s(s+4)(s+5)}$$

Characteristic equation, $1 + G(s)H(s) = 0$

$$\Rightarrow 1 + \frac{K}{s(s+4)(s+5)} = 0$$

$$\Rightarrow s(s+4)(s+5) + K = 0$$

$$\Rightarrow s^3 + 9s^2 + 20s + K = 0$$

$$\begin{array}{c|cc} s^3 & 1 & 20 \\ s^2 & 9 & K \\ s^1 & \frac{180-K}{9} & 0 \\ s^0 & K \end{array}$$

The system to be marginally stable, $180 - K = 0$

$$\Rightarrow K = 180$$

$$9s^2 + K = 0$$

$$\Rightarrow 9s^2 + 180 = 0$$

$$\Rightarrow s = \pm j\sqrt{20} = \pm j2\sqrt{5}$$

Q. 95) The special case of a finite-duration sequence is given as

$$x(n) = \left\{ 2, \underset{\uparrow}{4}, 0, 3 \right\}$$

The sequence x(n) into a sum of weighted impulse sequences will be

(a) $2\delta(n+1) + 4\delta(n) + 3\delta(n-2)$

(b) $2\delta(n) + 4\delta(n-1) + 3\delta(n-3)$


(c) $2\delta(n) + 4\delta(n-1) + 3\delta(n-2)$

(d) $2\delta(n+1) + 4\delta(n) + 3\delta(n-1)$

ANS: A

$$x(n) = \left\{ 2, \underset{\uparrow}{4}, 0, 3 \right\}$$

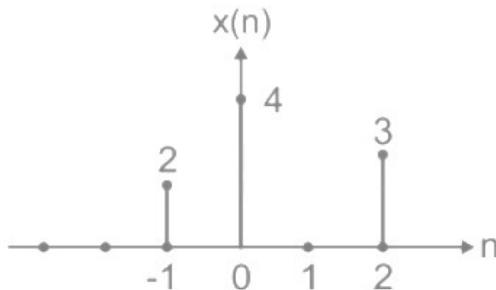The arrow indicates the origin. This can be represented as:



In terms of unit impulse sequences, this can be represented as:

$$x(n) = 2\delta(n + 1) + 4\delta(n) + 3\delta(n - 2)$$

Q. 96) _____ is also known as Hertz antenna

- (a) Concave plane antenna
- (b) Horn antenna
- (c) Parabolic reflector antenna
- (d) Half-wave dipole antenna

ANS: D

Hertz antenna is a dipole antenna of length equal to half of the wavelength of transmitted EM wave.

$$\therefore l = \frac{\lambda}{2} = \frac{\nu}{2f}$$

Q. 97) Which of the following is the CORRECT representation of transconductance?

(a) $G_M = I/V_i$

(b) $G_M = V/V_i$

(c) $G_M = I/I_i$

(d) $GM = V/I_i$

ANS: A

Q. 98) _____ is usually used in RF power amplifier and in amateur radio.

(a) Primary amplifier

(b) Secondary amplifier

(c) Non-linear amplifier

(d) Linear amplifier

ANS: D

Q. 99) The Fourier transform of a double sided exponential function $e^{-\frac{1}{2}|t|}$ is

(a) $\frac{2}{1 + 4\omega^2}$

(b) $\frac{1 + 4\omega^2}{4}$

(c) $\frac{1 + 4\omega^2}{2}$

(d) $\frac{4}{1 + 4\omega^2}$

ANS: D

For the given two-sided exponential:

$$x(t) = e^{-\frac{1}{2}|t|}$$

$$a = \frac{1}{2}$$

The Fourier transform from equation (1) will be:

$$e^{\frac{-1}{2}|t|} \leftrightarrow \frac{2 \times \frac{1}{2}}{\left(\frac{1}{2}\right)^2 + \omega^2}$$

$$e^{-\frac{1}{2}|t|} \leftrightarrow \frac{1}{\omega^2 + \frac{1}{4}}$$

$$e^{-\frac{1}{2}|t|} \leftrightarrow \frac{4}{1+4\omega^2}$$

Q. 100) TRAP is

- (a) Maskable, highest priority and software interrupt
- (b) Non-maskable, highest priority and hardware interrupt
- (c) Non-maskable, highest priority software interrupt
- (d) Maskable, lowest priority and hardware interrupt

ANS: B
